

Example

- Node Voltage Analysis

- Eg

P 4.3-3 Determine the values of the power supplied by each of the sources in the circuit shown in Figure P 4.3-3.


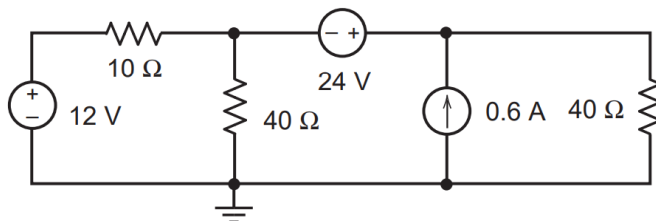


Figure P 4.3-3

- Superposition

-

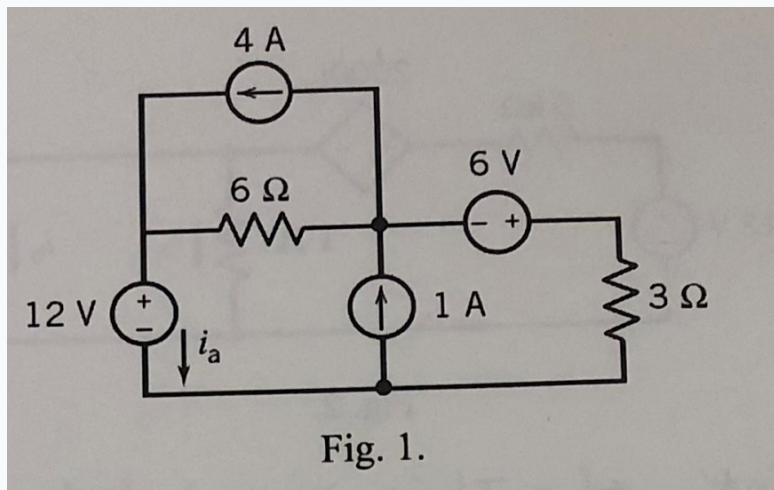

- Thevenin's Theorem

P 5.4-11 \oplus For the circuit of Figure P 5.4-11, specify the value of the resistance R_L that will cause current i_L to be -2 A.

Answer: $R_L = 12 \Omega$


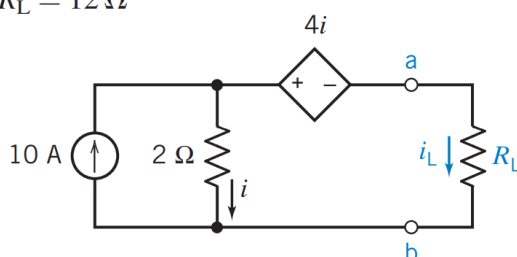



Figure P 5.4-11

- Answer

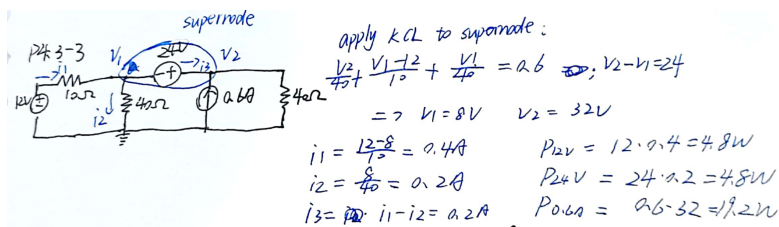- Q1: $P_{12} = 4.8W$; $P_{24} = 4.8W$; $P_{0.6} = 19.2W$;




• Q2: 1A

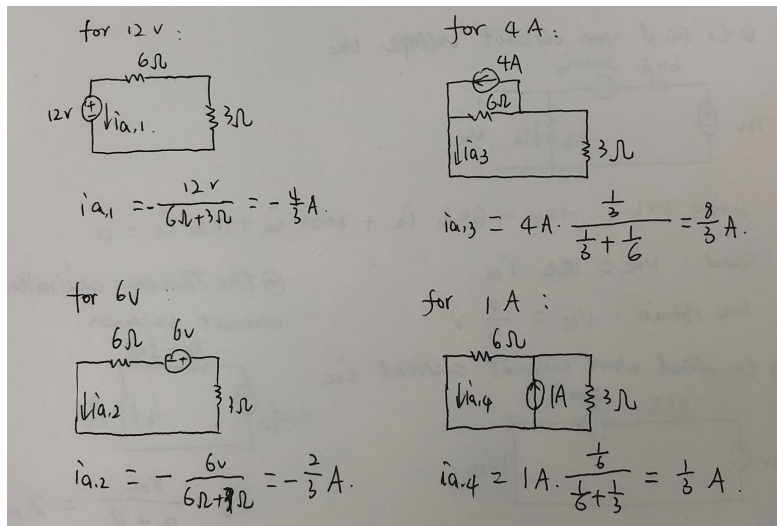

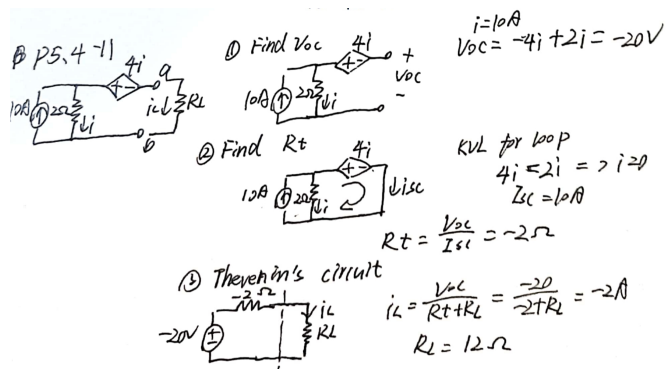• Q3: 12

- $V_{oc} = -20V$, $I_{sc} = 10A$; $R_t = -2\Omega$;



以上内容整理于 幕布文档